

Unit Name: Basics of wiring - Star and Delta Connections

Class: UG 3rd Semester, Physics Hons.

Paper: SEC1 (Electrical Circuits and Network Skills)

Dr. Jyotirmoy Pramanik

Department of Physics

Kharagpur College

Three phase AC Systems

R, Y, B


2 possible connections.

- ① Star (or) Y
 - ② Delta (or) Mesh
- } Governed by characteristics equation relating to I & V .

* phasor diagram play a vital role.

STAR CONNECTION

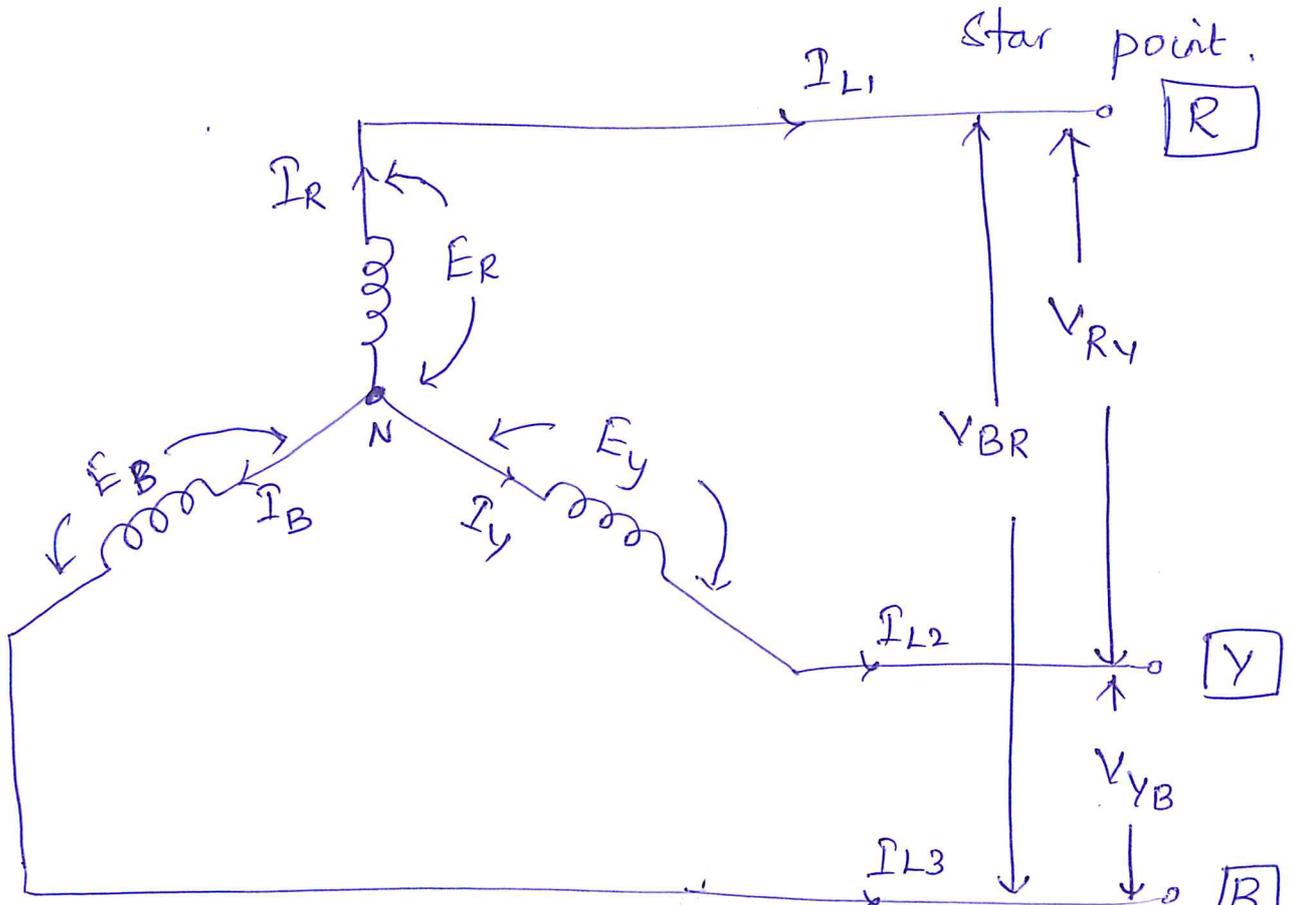- ↳ 3 similar ends are joined together
- ↳ common point
- ↳ Neutral point (or) Star point.



$I_R, I_Y, I_B \rightarrow$ Phase currents.

$I_{L1}, I_{L2}, I_{L3} \rightarrow$ line currents.

$E_R, E_Y, E_B \rightarrow$ Phase voltage.

$V_{RY}, V_{YB}, V_{BR} \rightarrow$ line voltage.

In a balanced system

$$E_R = E_Y = E_B = E_P$$

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

~~$$I_P = I_L$$~~

$$I_R = I_Y = I_B = I_P$$

$$I_{L1} = I_{L2} = I_{L3} = I_L$$


Apply KCL

$$I_R = I_{L1}$$

$$I_Y = I_{L2}$$

$$I_B = I_{L3}$$

Phase current = line current

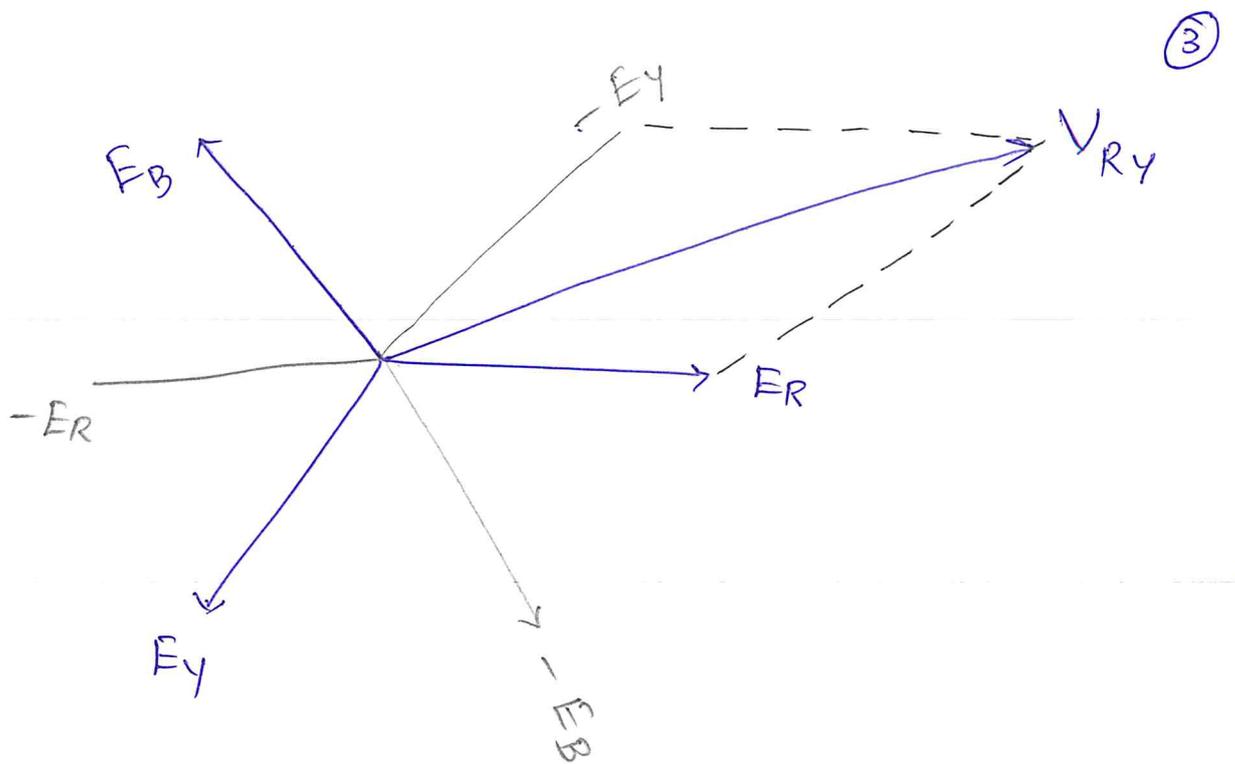

Apply KVL

$$E_R - E_Y = V_{RY}$$

$$\begin{aligned} V_{RY} &= \sqrt{E_R^2 + E_Y^2 + 2 E_R E_Y \cos 60^\circ} \\ &= \sqrt{E_p^2 + E_p^2 + 2 E_p E_p \cos 60^\circ} \\ &= \sqrt{3 E_p^2} \end{aligned}$$

$\downarrow \frac{1}{2}$

$$V_{RY} = \sqrt{3} E_p$$

Similarly

$$E_Y - E_B = V_{YB} \Rightarrow V_{YB} = \sqrt{3} E_p$$

$$E_B - E_R = V_{BR} \Rightarrow V_{BR} = \sqrt{3} E_p$$

Thus


(4)

$$V_L = \sqrt{3} E_p$$

line voltage = $\sqrt{3}$ phase voltage.

Phase voltage = $\frac{\text{Line voltage}}{\sqrt{3}}$

DELTA CONNECTION

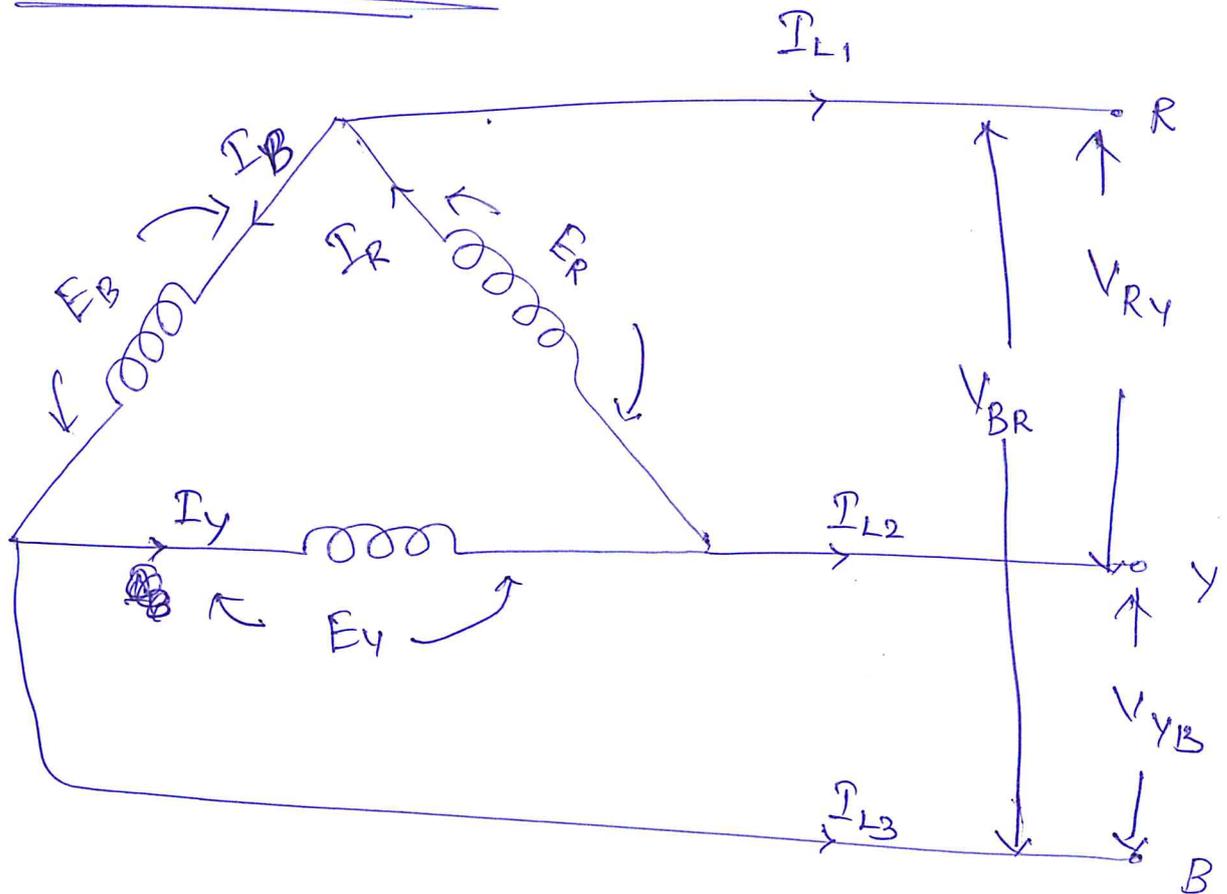

Dissimilar ends of 3 ϕ coils connected together. \rightarrow Delta Δ connection.

(5)

$E_R, E_Y, E_B \rightarrow$ Phase voltages

$I_R, I_Y, I_B \rightarrow$ Phase currents.

$I_{L1}, I_{L2}, I_{L3} \rightarrow$ Line current.

$V_{RY}, V_{YB}, V_{BR} \rightarrow$ Line voltage.

Δ_n Balanced system

$$E_R = E_Y = E_B = E_P$$

$$I_R = I_Y = I_B = I_P$$

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

$$I_{L1} = I_{L2} = I_{L3} = I_L$$

Apply KVL


$$E_R = V_{RY}$$

$$E_Y = V_{YB}$$

$$E_B = V_{BR}$$

Phase voltage = Line voltage.

6

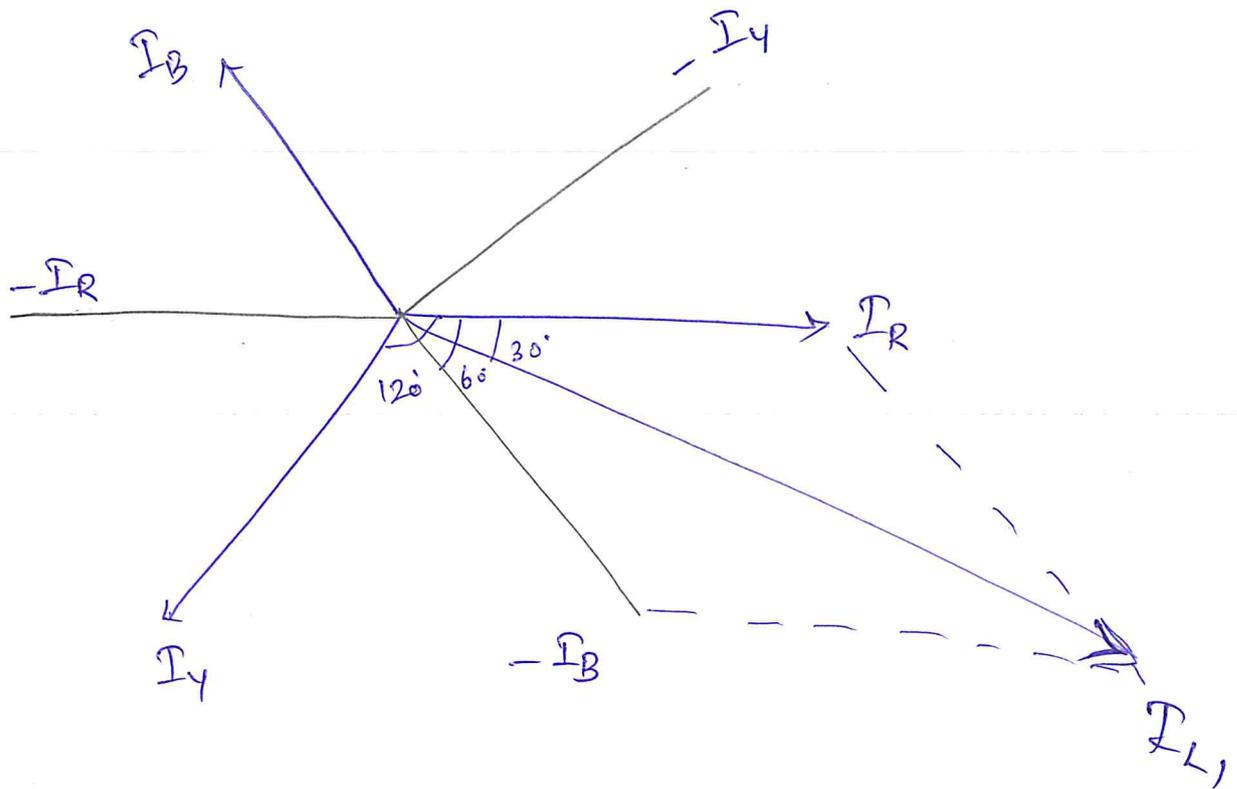

$$I_{L1} = \sqrt{I_R^2 + I_B^2 + 2 I_R I_B \cos 60^\circ}$$
$$= \sqrt{I_p^2 + I_p^2 + 2 I_p I_p \cos 60^\circ}$$

$$I_{L1} = I_p \sqrt{3}$$

Similarly

$$I_Y - I_R = I_{L2} \Rightarrow I_{L2} = \sqrt{3} I_p$$

$$I_B - I_Y = I_{L3} \Rightarrow I_{L3} = \sqrt{3} I_p$$

$$I_L = \sqrt{3} I_p$$

Line current = $\sqrt{3}$ Phase current

$$\text{Phase current} = \frac{\text{Line current}}{\sqrt{3}}$$

Power relationship. $\hookrightarrow \cos \phi \rightarrow \text{PF}$.

(7)

$$\text{Power / phase} = E_{ph} I_{ph} \cos \phi.$$

$$\text{Total power in all 3 phases} = 3 E_{ph} I_{ph} \cos \phi.$$

Star

$$\text{Total power} = 3 E_p I_p \cos \phi.$$

$$P = 3 \frac{V_L}{\sqrt{3}} I_L \cos \phi$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

Delta

$$\text{Total power} = 3 E_p I_p \cos \phi$$

$$= 3 V_L \frac{I_L}{\sqrt{3}} \cos \phi$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

Similarly.

$$\text{Total reactive power} = \sqrt{3} V_L I_L \sin \phi$$

$$\text{Total Apparent power} = \sqrt{3} V_L I_L$$

Comparison between Star and Delta Connections

Star and Delta Connections are the two types of connections in a 3 – phase circuits. A Star Connection is a 4 – wire system and a Delta Connection is a 3 – wire system.

Before going in to details of the Star Connection, Delta Connection and comparing those two, let us have a very brief note on three – phase electric power.

A single phase system consists of just two conductors (wires): one is called the phase, through which the current flows and the other is called neutral, which acts as a return path to complete the circuit.


In a three – phase system, we have a minimum of three conductors or wires carrying AC voltages. It is more economical to transmit power using a 3 – phase power supply when compared to a single phase power supply as a three – phase supply can transmit three time the power with three conductors when compared to a two – conductor single – phase power supply.

Hence, most of the power generated and distributed is actually a 3 – phase power (but majority of households will receive a single phase supply).


Further, the three – phase electric power system can be arranged in two ways. They are: [Star \(also called Y or Wye\) and Delta \(\$\Delta\$ \)](#).

Star Connections are mainly required for the Power Transmission Network for longer distances, whereas in **Delta connection** mainly in Distribution networks and is used for shorter distances. In **Star Connection**, each winding receives 230 volts and in **Delta Connection**, each winding receives 415 volts.

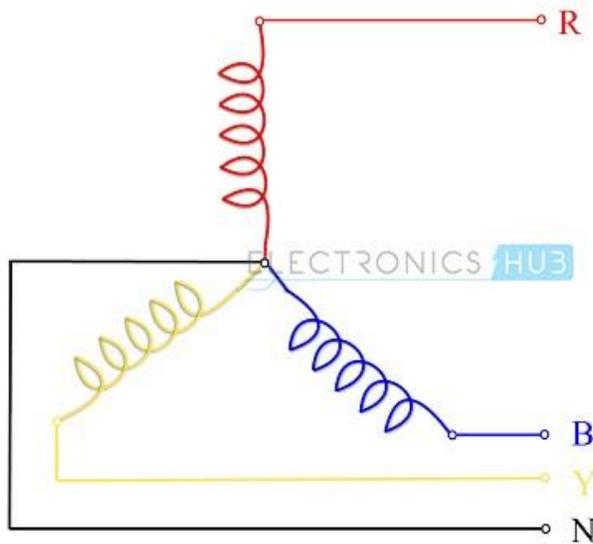In a Star Connection, there are 4 wires: 3 phase wires and 1 neutral wire whereas in a Delta Connection, there are only 3 wires for distribution and all the 3 wires are phases (no neutral in a Delta connection). The following image shows a typical Star and Delta Connection.



Star Connection (Y or WYE)

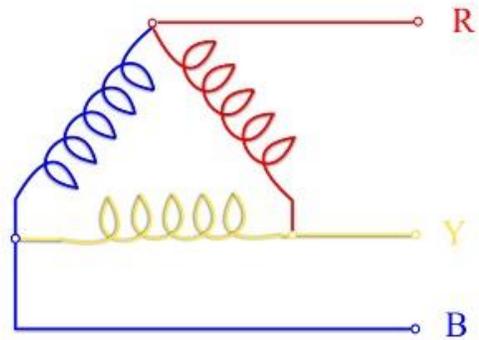

Delta Connection (Δ)

Let us understand more about these connections by using the following Comparison between Star and Delta Connections.

STAR CONNECTION (Y OR WYE)	DELTA CONNECTION (Δ)
A Star Connection is a 4 – wire connection (4th wire is optional in some cases)	A Delta Connection is a 3 – wire connection.
Two types of Star Connection systems are possible: 4 – wire, 3 – phase system and 3 – wire 3 phase system.	In Delta Connection, only 3 – wire 3 phase system is possible.

<p>Out of the 4 wires, 3 wires are the phases and 1 wire is the neutral (which is the common point of the 3 wires).</p>	<p>All the 3 wires are phases in a Delta Connection.</p>
<p>In a Star Connection, one end of all the three wires are connected to a common point in the shape of Y, such that all the three open ends of the three wires form the three phases and the common point forms the neutral.</p>	<p>In a Delta Connection, every wire is connected to two adjacent wires in the form of a triangle (Δ) and all the three common points of the connection form the three phases.</p>
<p>The Common point of the Star Connection is called Neutral or Star Point.</p>	<p>There is no neutral in Delta Connection</p>
<p>Line Voltage (voltage between any two phases) and Phase Voltage (voltage between any of the phase and neutral) is different.</p>	<p>Line Voltage and Phase Voltage are same.</p>
<p>Line Voltage is root three times phase voltage i.e. $V_L = \sqrt{3} V_P$. Here, V_L is Line Voltage and V_P is Phase Voltage.</p>	<p>Line Voltage is equal to Phase Voltage i.e. $V_L = V_P$.</p>

<p>With a Star Connection, you can use two different voltages as V_L and V_P are different. For example, in a 230V/400V system, the voltage between any of the phase wire and neutral wire is 230V and the voltage between any two phases is 400V.</p>	<p>In a Delta Connection, we get only a single voltage magnitude.</p>
<p>Line Current and Phase Current are same.</p>	<p>Line current is root three times the phase current.</p>
<p>In Star Connection, $I_L = I_P$. Here, I_L is line current and I_P is phase current.</p>	<p>In Delta connection, $I_L = \sqrt{3} I_P$</p>
<p>Total three phase Power in a Star Connection can be calculated using the following formulae.</p> <p>$P = 3 \times V_P \times I_P \times \cos(\Phi)$ or</p> <p>$P = \sqrt{3} \times V_L \times I_L \times \cos(\Phi)$</p>	<p>Total three phase Power in a Delta Connection can be calculated using the following formulae.</p> <p>$P = 3 \times V_P \times I_P \times \cos(\Phi)$ or</p> <p>$P = \sqrt{3} \times V_L \times I_L \times \cos(\Phi)$</p>

<p>Since Line Voltage and Phase Voltage are different ($V_L = \sqrt{3} V_P$), the insulation required for each phase is less in a Star Connection.</p>	<p>In a Delta Connection, the Line and Phase Voltages are same and hence, more insulation is required for individual phases.</p>
<p>Usually, Star Connection is used in both transmission and distribution networks (with either single phase supply or three – phase).</p>	<p>Delta Connection is generally used in distribution networks.</p>
<p>Since insulation required is less, Star Connection can be used for long distances.</p>	<p>Delta Connections are used for shorter distances.</p>
<p>Star Connections are often used in application which require less starting current</p>	<p>Delta Connections are often used in applications which require high starting torque.</p>